




LearnOBots

Think Explore Make

SOLAR HOUSE

2

Connecting a FAN

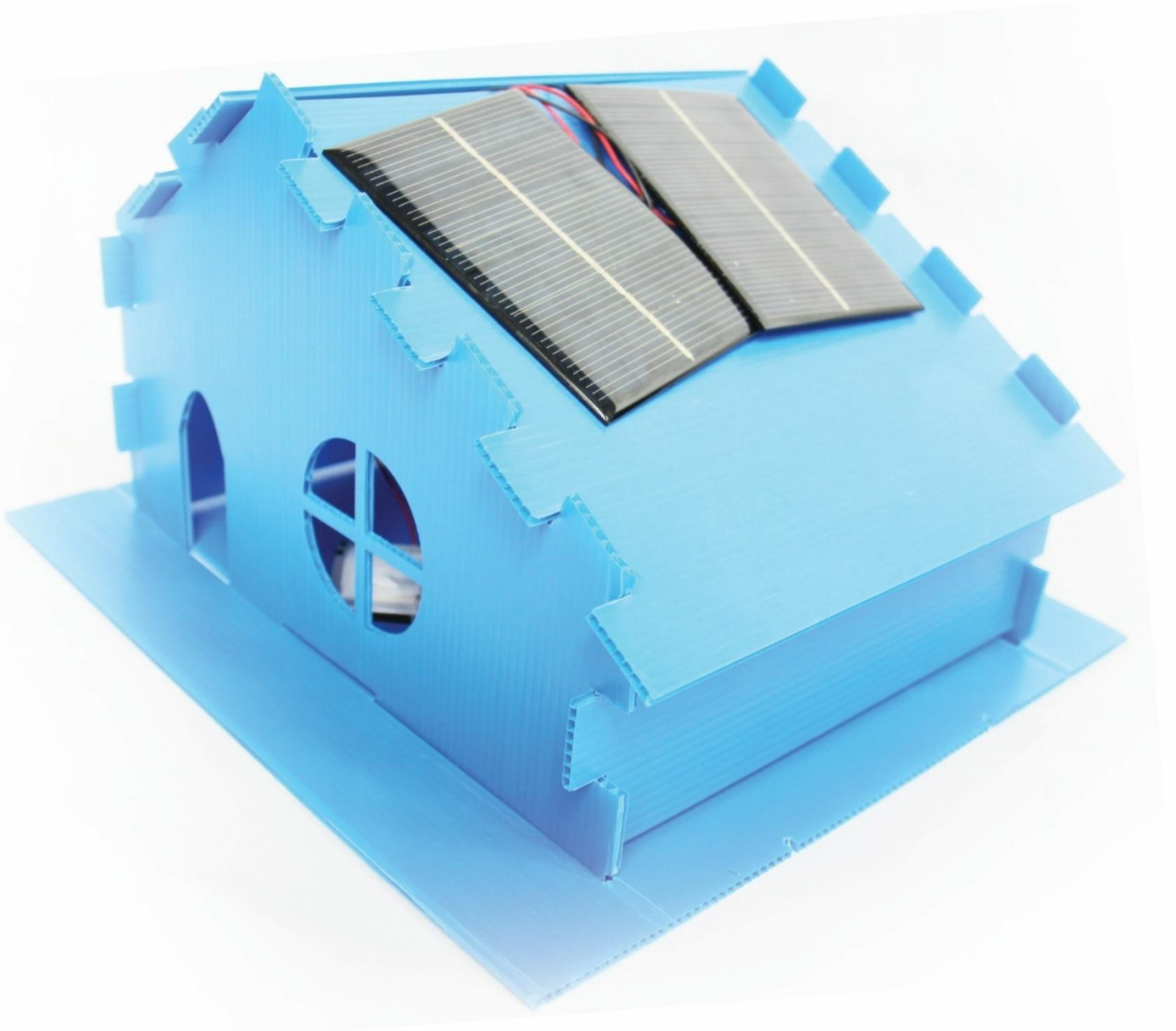


Connecting a Fan

I want to add a fan to my solar house




I have the circuit Diagram

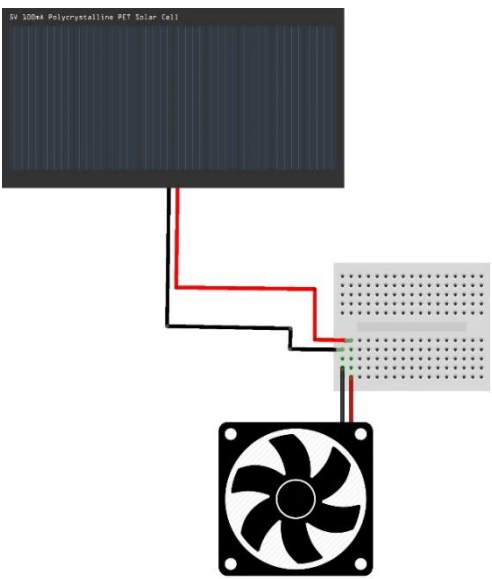

But this is a little bit confusing....


1

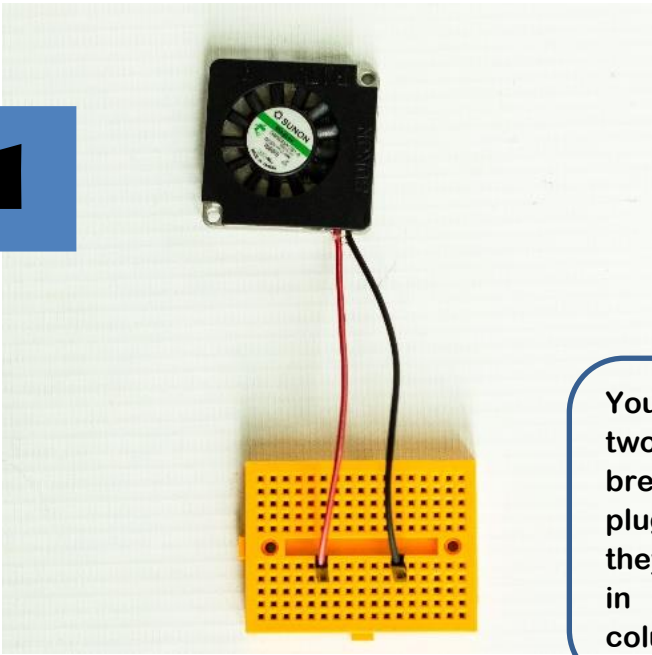

You can use any two holes of the bread board to plug in the fan but they should not be in the same column vertically.

Insert the red and black wires of the fan into the bread board


2

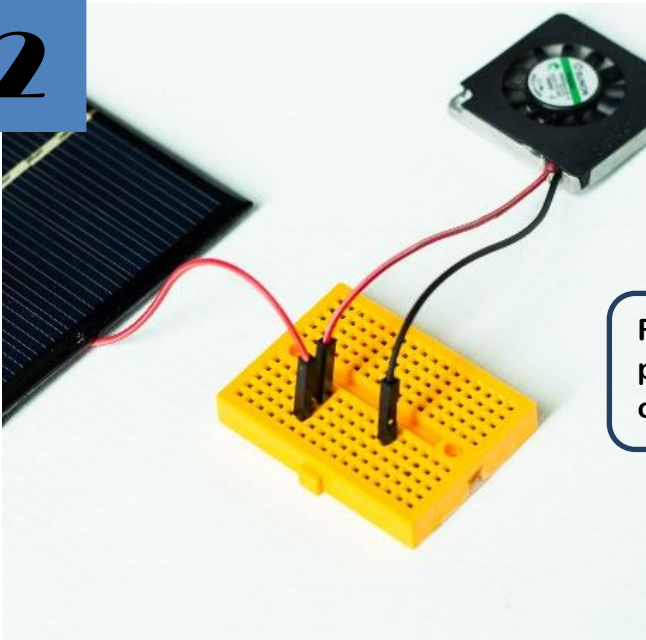

Red wire of solar panel in the same column vertically

Now connect the red wire of the solar panel in the same column as the red wire of the fan

3

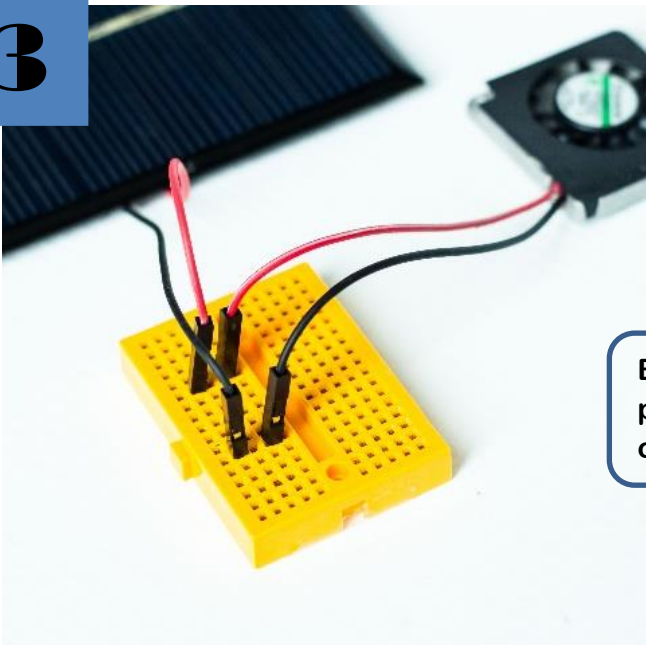

Black wire of solar panel in the same column vertically

Connect the black wire of the fan with black wire of solar panel