




LearnOBots  
Think Explore Make


# SOLAR HOUSE

3

CONNECTING AN LED & FAN  
TOGETHER

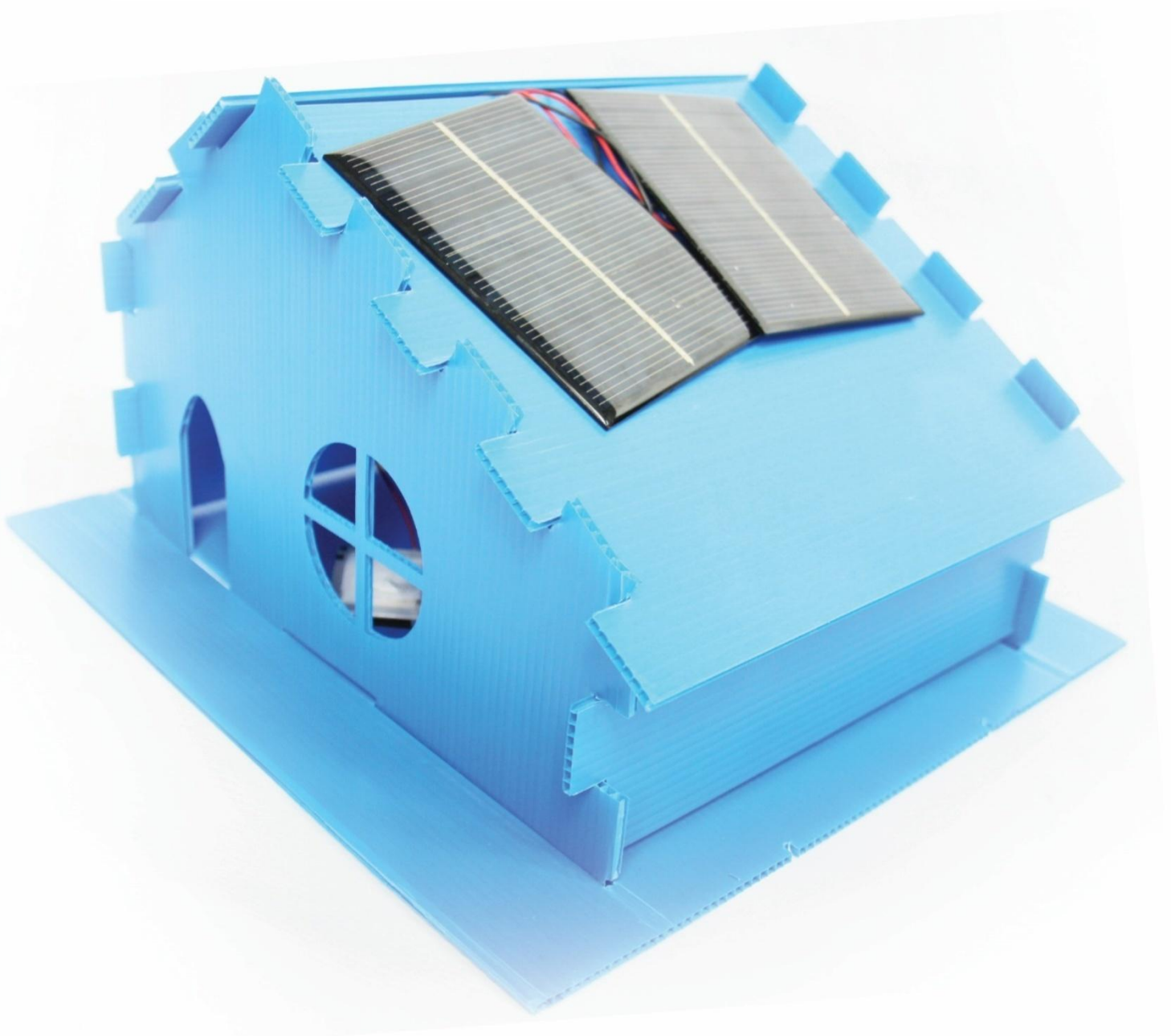

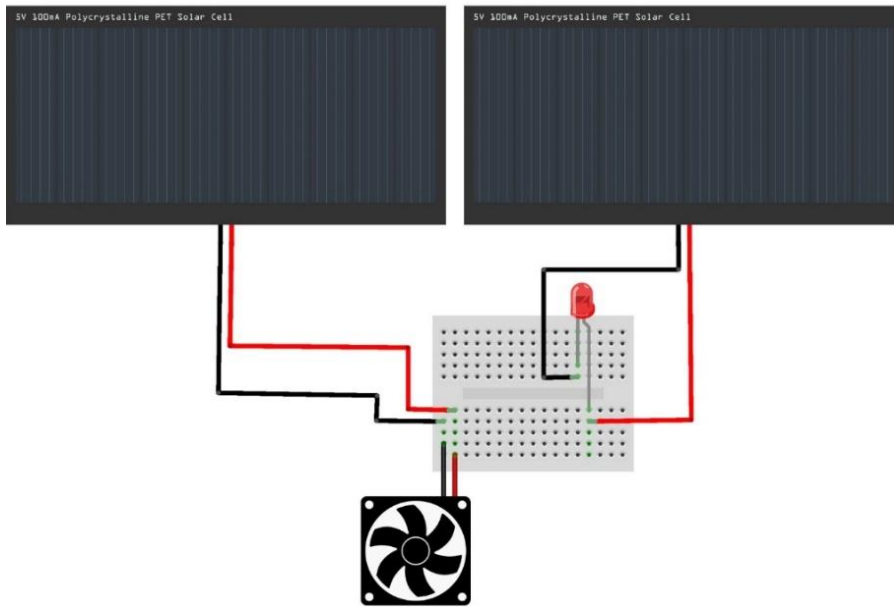
# Let's connect an LED and a Fan together



We have the circuit diagram

fritzing

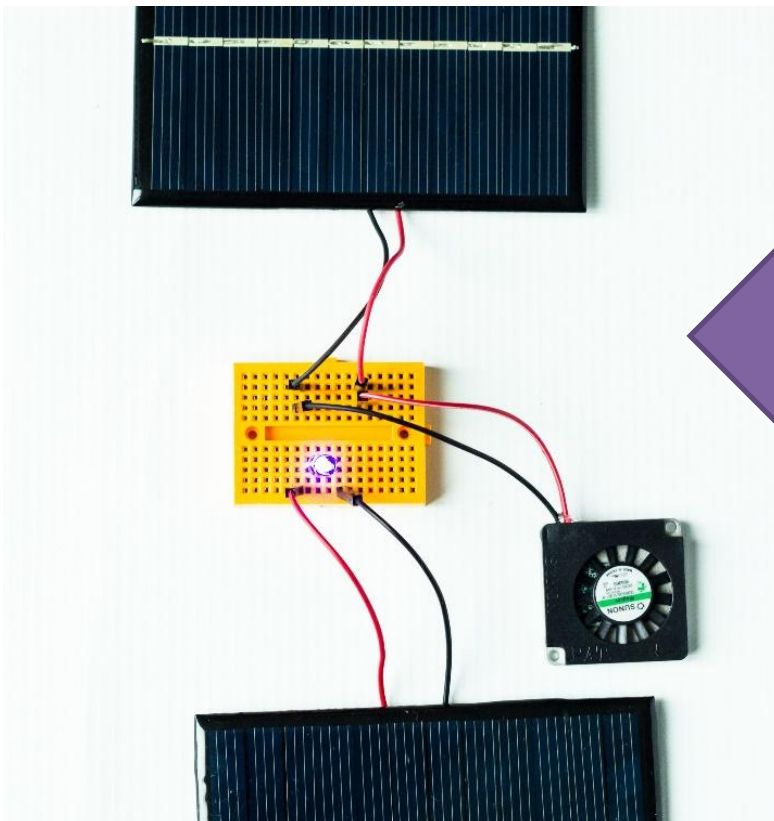

Following the above mentioned steps we can connect both LED and fan with a single bread board