




LearnOBots
Think Explore Make

SOLAR HOUSE


9

DOOR BELL

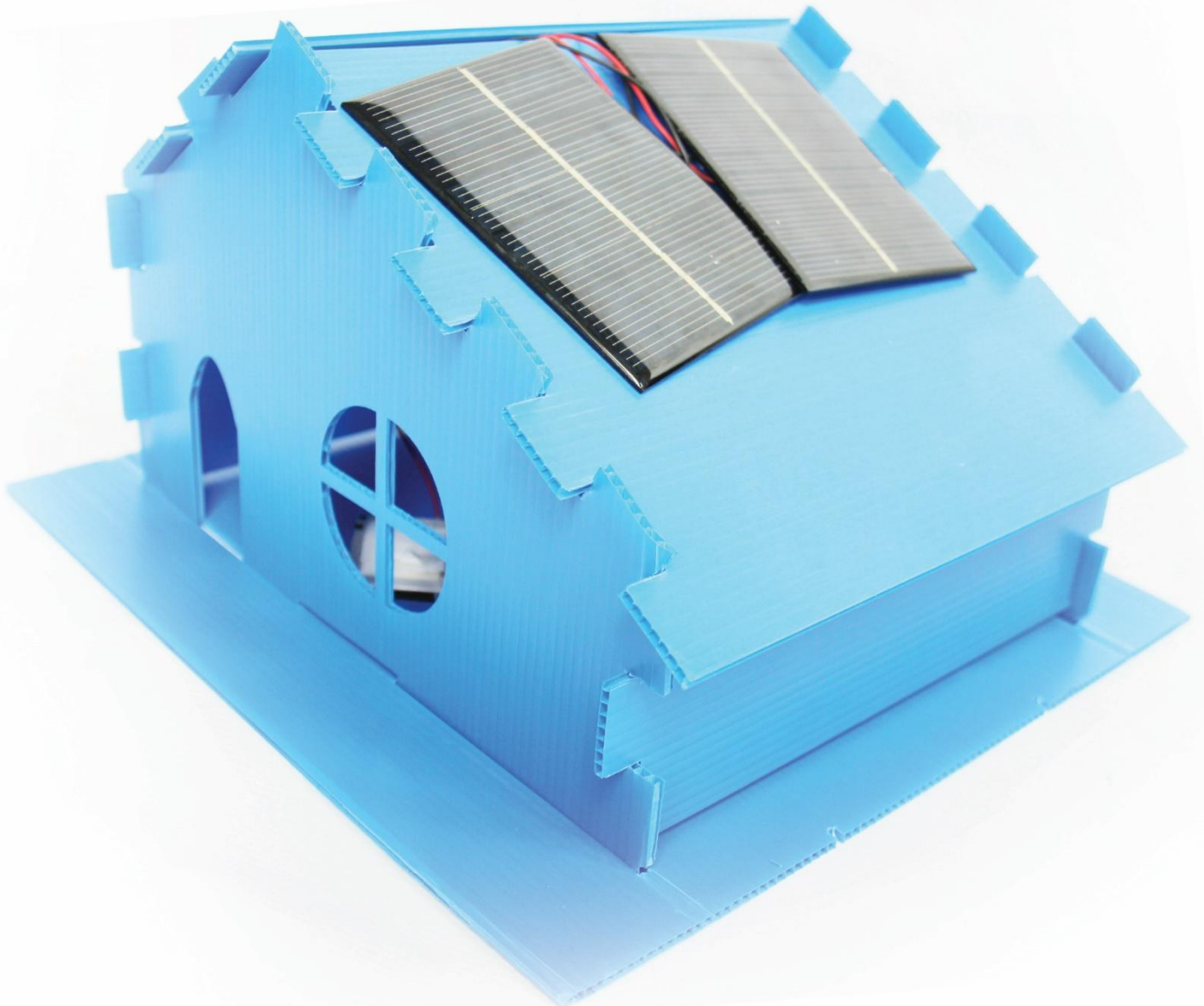


Activity Manual for Solar House


1. Take a bread board.

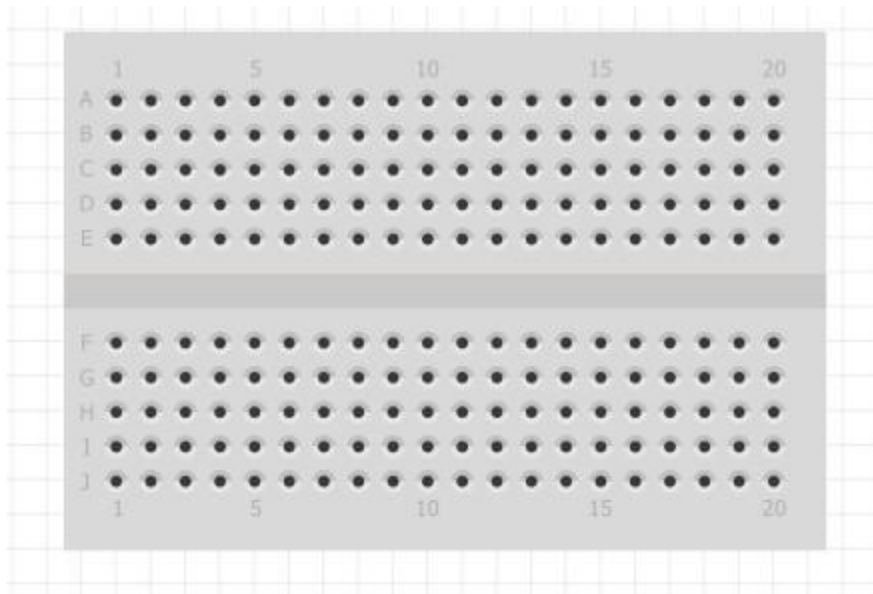


2. Attach a Solar Panel as shown.

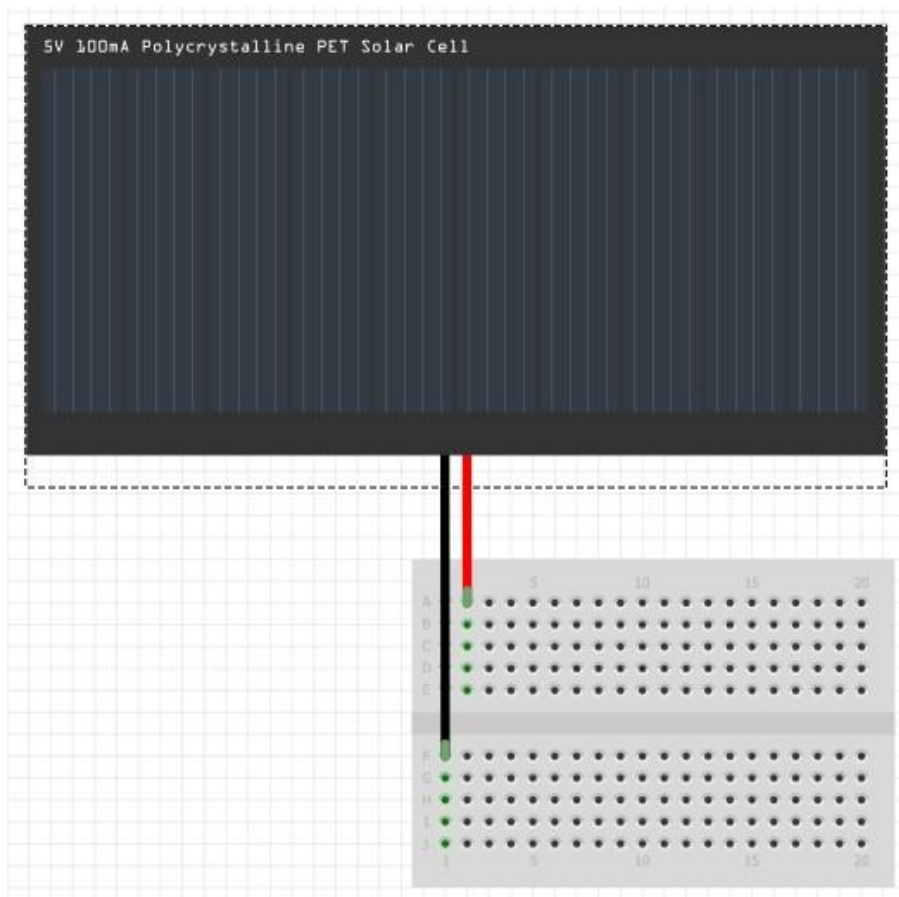


3. Attach a Push button as shown.

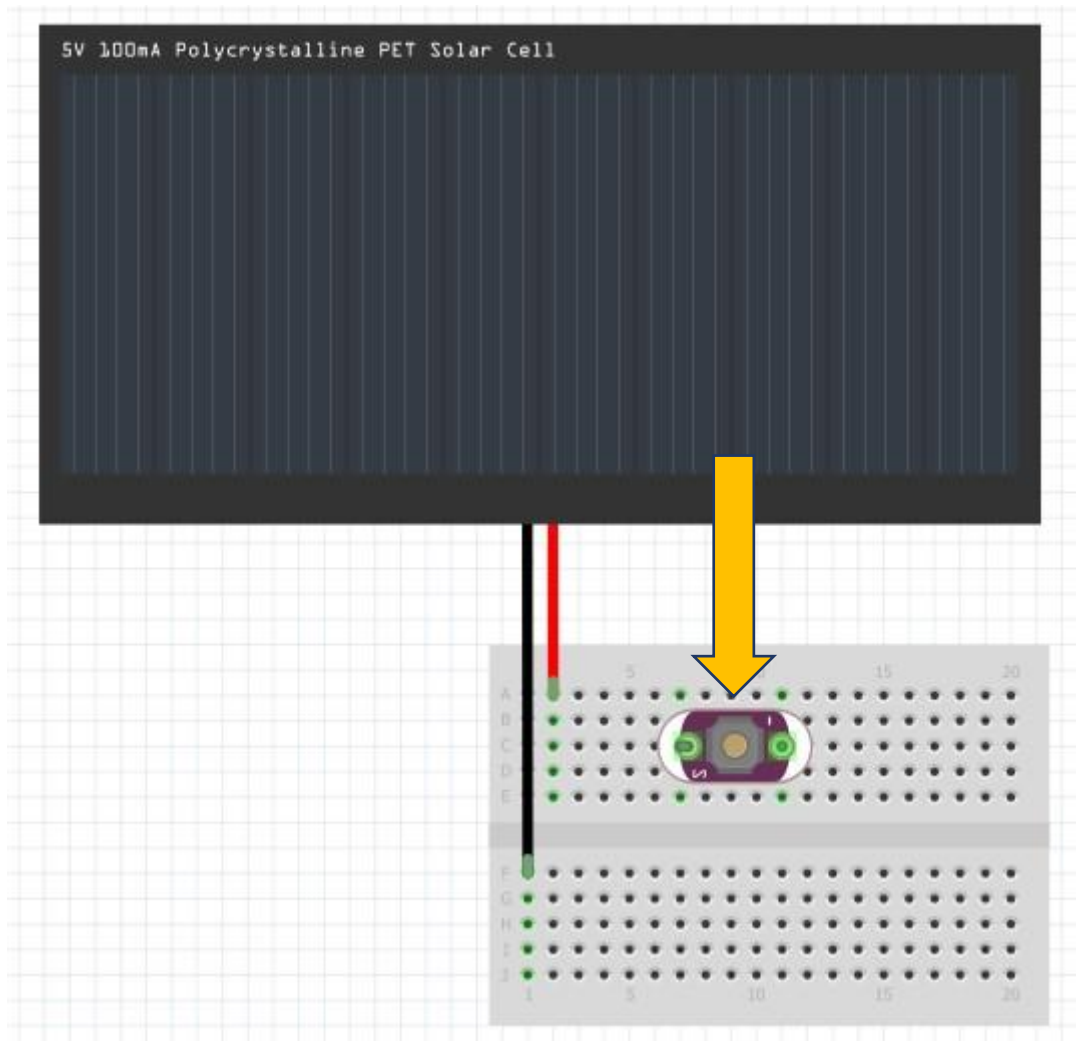


4. Make connection as shown.

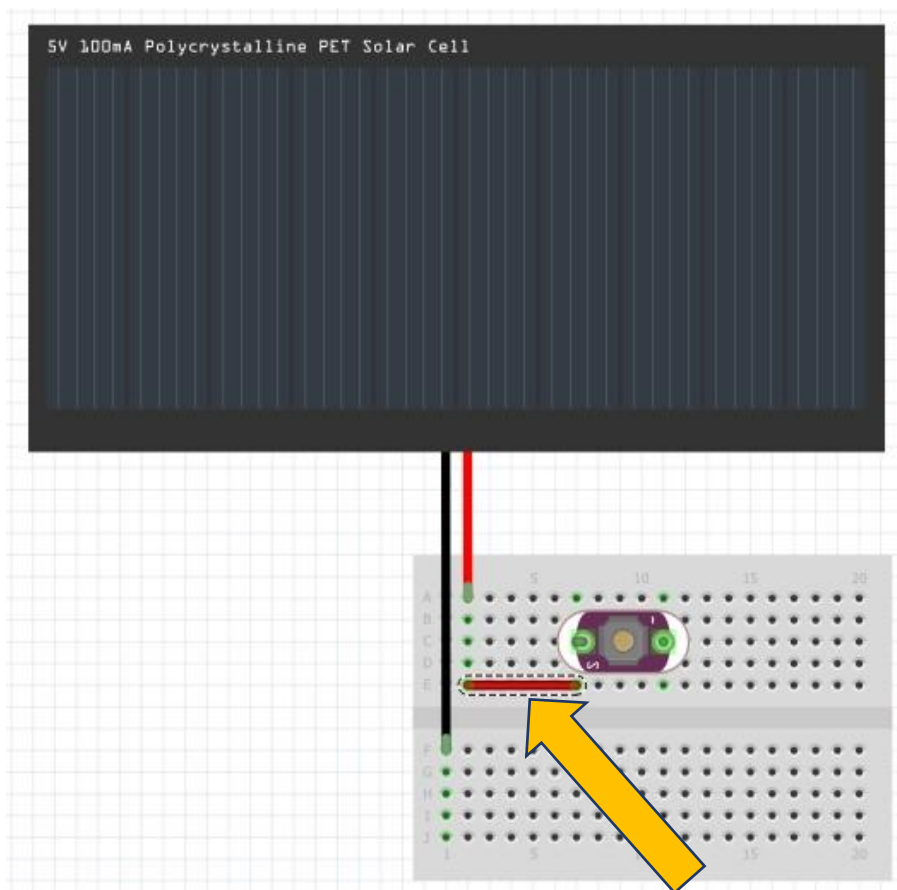


5. Connect the buzzer as shown.

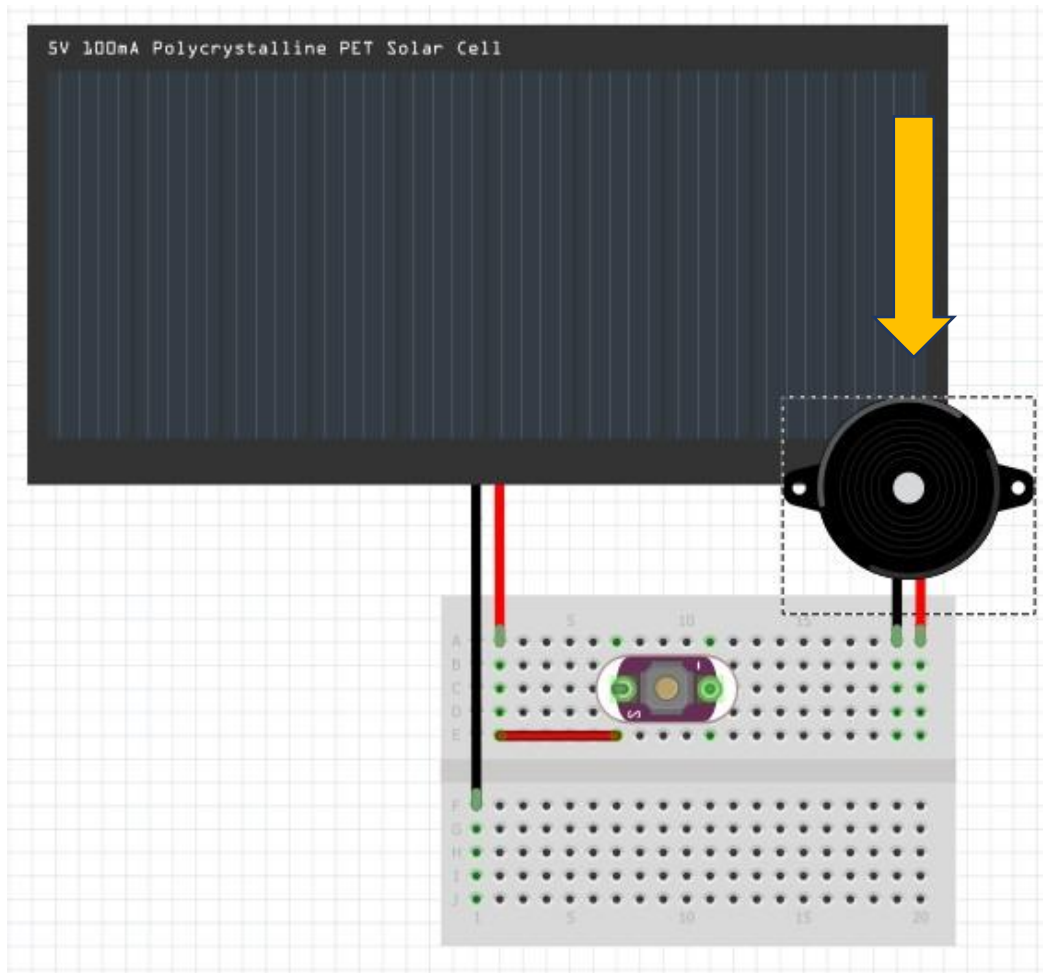


6. Attach the connecting wire as shown.

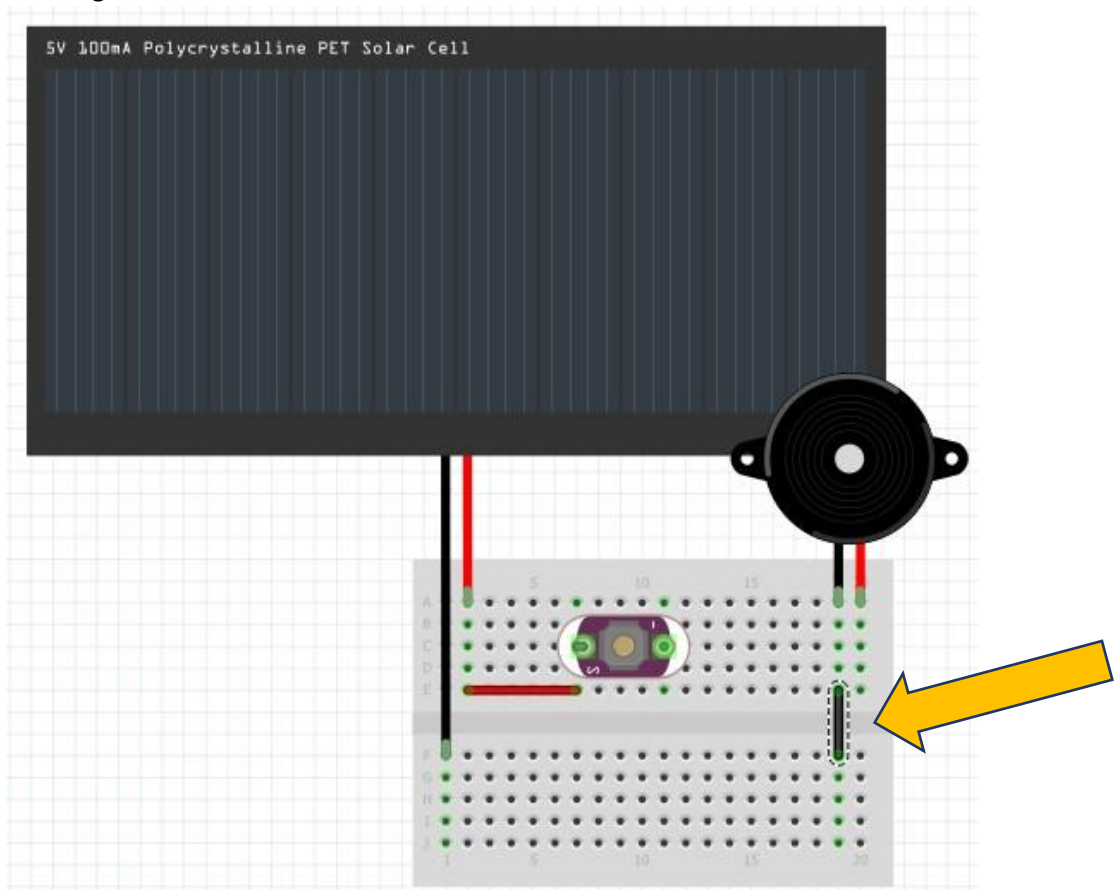

7. Attach the connecting wire as shown.

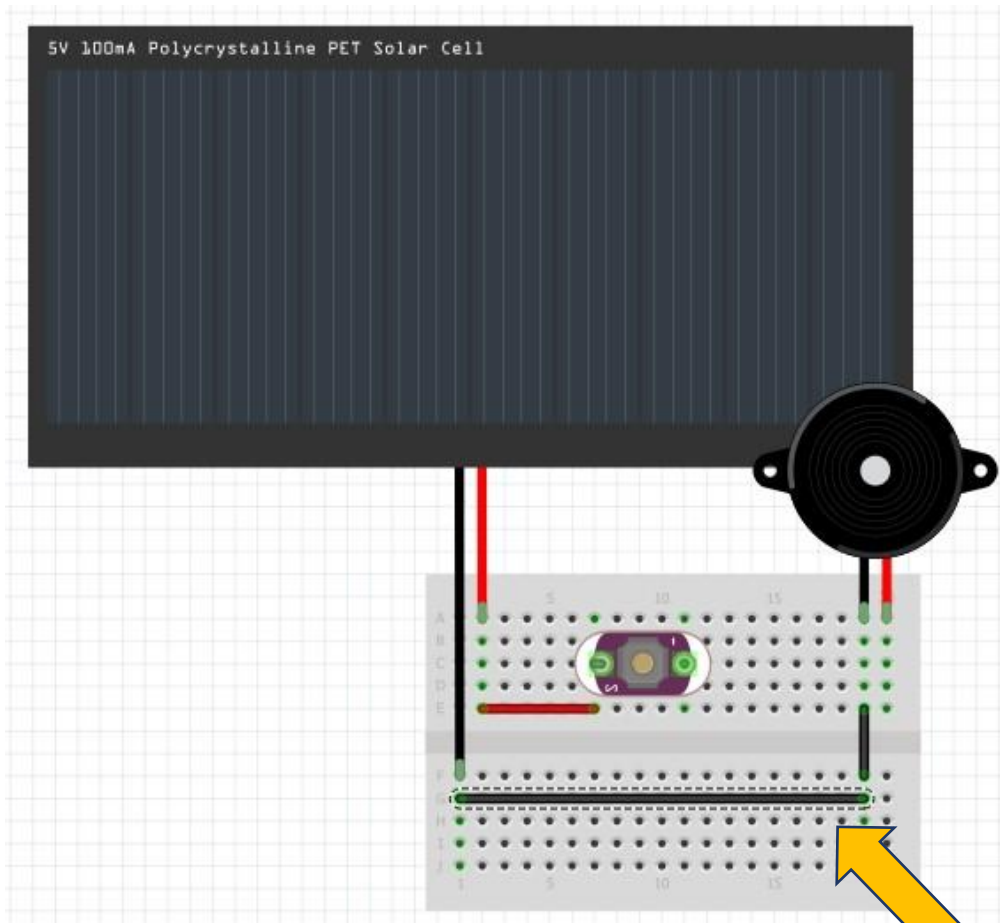

8. Make connection as shown.

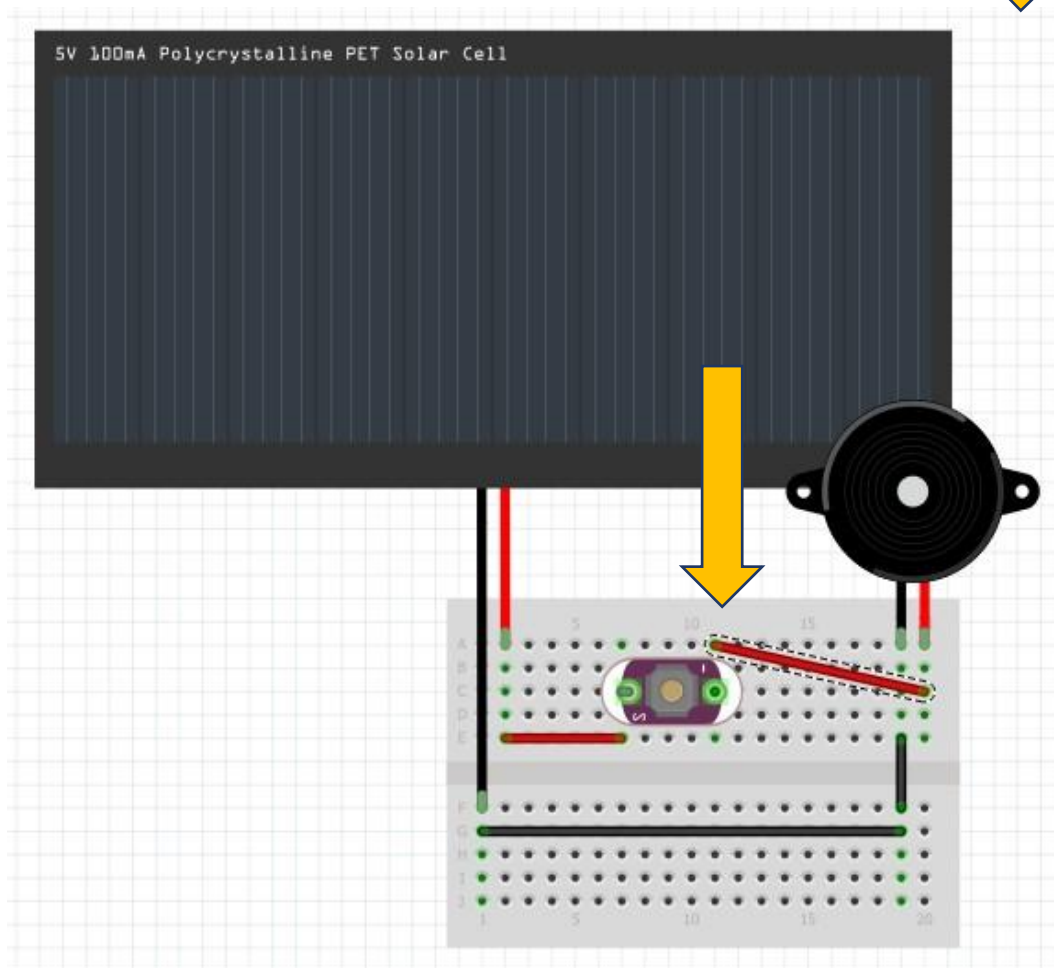

9. Your circuit is now complete.

10. Push the Button to Buzz the Buzzer.

NOTE: Since this activity involves a solar panel as its source of energy, so it will only work when the panel is placed in broad daylight